



Timing diagram for a 4-bit ripple-carry adder. The diagram shows three 4-bit data buses (A, B, and Sum) and a carry-in signal over a 1000 ns period. A is 0011, B is 0001, and the resulting Sum is 0100. The carry-in is high for the first 320 ns and then low.